


Lecture 3 : Gate-Level Minimization

Outline

- ❑ four-variable Karnaugh Map
- ❑ NAND and NOR Implementations
- ❑ Other Two-Level Implementations
- ❑ Exclusive-OR Function

Four-Variable Maps

YZ WX				
	00	01	11	10
00	m_0	m_1	m_3	m_2
01	m_4	m_5	m_7	m_6
11	m_{12}	m_{13}	m_{15}	m_{14}
10	m_8	m_9	m_{11}	m_{10}

 

- Top cells are adjacent to bottom cells. Left-edge cells are adjacent to right-edge cells.
- Note variable ordering (WXYZ).

Example

- Simplify the following Boolean function $(A,B,C,D) = \sum m(0,1,2,4,5,7,8,9,10,12,13)$.
- First put the function $g()$ into the map, and then group as many 1s as possible.

cd
ab

1	1		1
1	1	1	
1	1		
1	1		1


1	1		1
1	1	1	
1	1		
1	1		1

$$g(A,B,C,D) = c' + b'd' + a'bd$$

 EXAMPLE 3.5

Simplify the Boolean function

$$F(w, x, y, z) = \Sigma(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$$




$$F = y' + w'z' + xz'$$

EXAMPLE 3.6

Simplify the Boolean function

$$F = A'B'C' + B'CD' + A'BCD' + AB'C'$$

 

$$F = B'D' + B'C' + A'CD'$$

Example

- Simplify the function $f(a,b,c,d)$ whose K-map is shown at the right.
- $f = a'c'd + ab' + cd' + a'bc'$
or
- $f = a'c'd + ab' + cd' + a'bd'$
- The middle two terms are EPIs, while the first and last terms are selected to cover the minterms m_1, m_4 , and m_5 .
- (There's a third solution!)

ab \ cd	00	01	11	10
00	0	1	0	1
01	1	1	0	1
11	0	0	x	x
10	1	1	x	x


0	1	0	1
1	1	0	1
0	0	x	x
1	1	x	x

0	1	0	1
1	1	0	1
0	0	x	x
1	1	x	x

 EXAMPLE 3.7

Simplify the following Boolean function into (a) sum-of-products form and (b) product-of-sums form:

$$F(A, B, C, D) = \Sigma(0, 1, 2, 5, 8, 9, 10)$$




(b) $F = (A' + B')(C' + D')(B' + D)$

Two Gate Implementations


- ❑ Sometimes product-of-sums representations may have smaller implementations

7 literals, 4 gates

 

$$(a) F = B'D' + B'C' + A'C'D$$

6 literals, 4 gates

 

$$(b) F = (A' + B')(C' + D')(B' + D)$$

Don't Care Conditions

- ❑ X = don't care (can be 0 or 1)
- ❑ Don't cares can be included to form a larger cube, but not necessary to be completely covered
- ❑ Ex: $F(w, x, y, z) = \Sigma(1,3,7,11,15)$ $d(w, x, y, z) = \Sigma(0,2,5)$

		y			
	yz	00	01	11	10
$w'x'$	00	m_0 X	m_1 1	m_3 1	m_2 X
	01	m_4 0	m_5 X	m_7 1	m_6 0
w	11	m_{12} 0	m_{13} 0	m_{15} 1	m_{14} 0
	10	m_8 0	m_9 0	m_{11} 1	m_{10} 0
		z			



(a) $F = yz + w'x'$

		y			
	yz	00	01	11	10
$w'z$	00	m_0 X	m_1 1	m_3 1	m_2 X
	01	m_4 0	m_5 X	m_7 1	m_6 0
w	11	m_{12} 0	m_{13} 0	m_{15} 1	m_{14} 0
	10	m_8 0	m_9 0	m_{11} 1	m_{10} 0
		z			

  (b) $F = yz + w'z$



NAND and NOR Implementation

- ❑ Digital circuits are frequently constructed with **NAND** or **NOR gates rather than with AND and OR gate**
 - ❑ NAND and NOR gates are much easier to fabricate
- ❑ NAND or NOR gates are both universal gates
 - ❑ Any digital system can be implemented with only NAND gates or NOR gates






Alternative Graphic Symbols

  - ❑ To facilitate the conversion to NAND or NOR logic, it is convenient to define alternative graphic symbols
 - ❑ “Bubble” means complement



Two-Level Implementation (NAND)

- ❑ It's easy to implement a Boolean function with only NAND gates if converted from a **sum of products form**
- ❑ Ex: $F = AB + CD = ((AB)'(CD)')'$

   




EXAMPLE 3.9

Implement the following Boolean function with NAND gates:

$$F(x, y, z) = \Sigma(1, 2, 3, 4, 5, 7)$$


Procedures:

   1. Simplify the function in sum of products
2. Draw NAND gates for the first level
3. Draw a single AND-invert or invert-OR in the second level
4. Add an inverter at the first level for the term with a single literal





Two-Level Implementation (NOR)

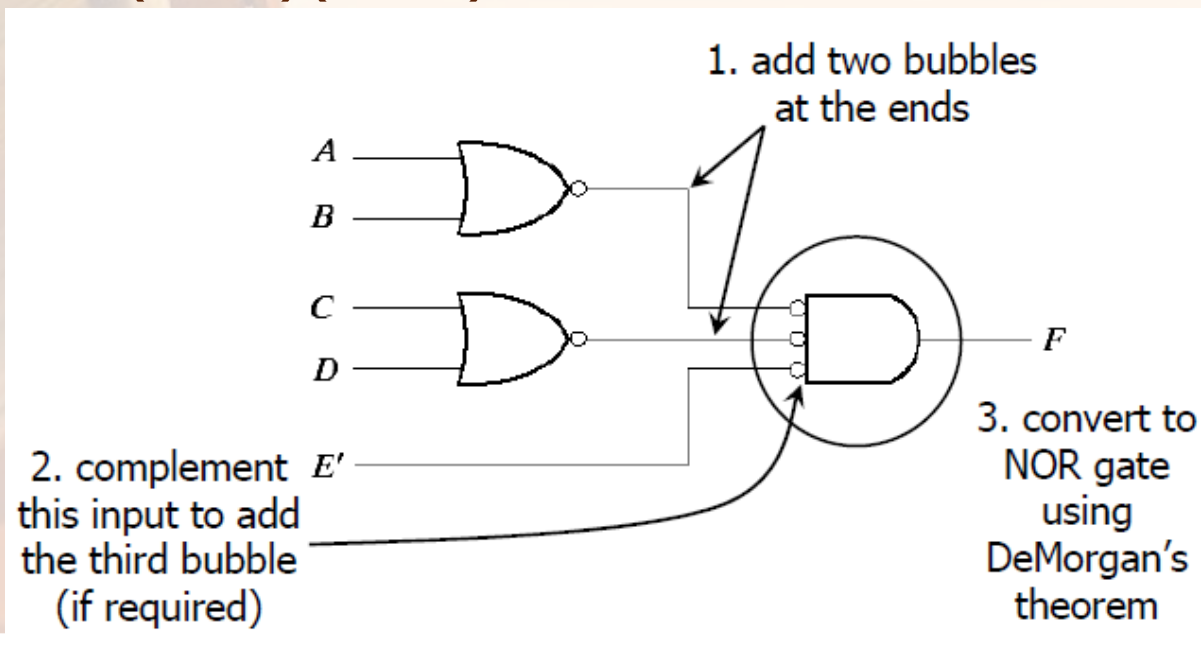- ❑ It's easy to implement a Boolean function with only NOR gates if converted from a **product of sums form**
- ❑ Ex: $F = (A+B)(C+D)E$



Multilevel NAND Circuits

Implementing $F = (AB' + A'B)(C + D')$

  


□ Procedures:

1. Convert all AND gates to NAND gates with AND-invert symbols
2. Convert all OR gates to NAND gates with invert-OR symbols
3. Check all bubbles and insert an inverter for the bubble that are not compensated by another bubble


Exclusive-OR (XOR) Function

- ❑ XOR is often denoted by the symbol \oplus
- ❑ Logic operation of XOR
 - ❑ $X \oplus Y = XY' + X'Y$
 - ❑ Equal to 1 if **only x is equal to 1 or if only y is equal to 1**, but not when both are equal to 1
- ❑ It's complement, exclusive-NOR (XNOR), is often denoted by the symbol \odot
- ❑ Logic operation
 - ❑ $X \odot Y = XY + X'Y'$
 - ❑ It is equal to 1 if **both x and y are equal to 1 or if both are equal to 0**
- ❑ Seldom used in general Boolean functions
 - ❑ Particularly useful in arithmetic operations and error detection and correction circuits

Exclusive-OR Implementations

 

(a) Exclusive-OR with AND-OR-NOT gates

 


(b) Exclusive-OR with NAND gates

Odd Function


❑ The multiple-variable XOR operation is defined as an **odd function**

❑ TRUE when no. of "1" in inputs is odd

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

 

(a) 3-input odd function

 


(a) Odd function $F = A \oplus B \oplus C$

Even Function

- ❑ The multiple-variable XNOR operation is defined as an **even function**
 - ❑ TRUE when no. of "1" in inputs is even

A	B	C	F
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

 

(b) 3-input even function

		<i>BC</i>		<i>B</i>	
		00	01	11	10
<i>A</i>	0	1		1	
	1		1		1
		<i>C</i>			

(a) Even function
 $F = (A \oplus B \oplus C)'$

Parity Generation and Checking


- ❑ An extra **parity bit is often added and** checked at the receiving end for error
- ❑ The circuit that generates the parity bit in the transmitter is called a **parity generator**
- ❑ The circuit that checks the parity in the receiver is called a **parity checker**
- ❑ Exclusive-OR functions are very useful to construct such circuits

Parity Generator

- ❑ For even parity:
- ❑ The total number of "1" (including P) is even
- ❑ The number of "1" at inputs is odd
- ❑ Generated with an **XOR** gate (odd function)
- ❑ $P = x \oplus y \oplus z$ (for 3-bit message)
- ❑ Similarly, odd parity can be generated with an XNOR gate

Table 3.3
Even-Parity-Generator Truth Table

Three-Bit Message			Parity Bit
<i>x</i>	<i>y</i>	<i>z</i>	<i>P</i>
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

 


(a) 3-bit even parity generator

$$P = x \oplus y \oplus z$$

Parity Checker

 - ❑ For even parity, the total number of "1" in the message is even
 - ❑ An error occurs when the received number of "1" is odd
- ❑ An XOR gate (odd function) can detect such an error
 - ❑ Has $n+1$ inputs



(b) 4-bit even parity checker

Table 3.4
Even-Parity-Checker Truth Table

Four Bits Received				Parity Error Check
<i>x</i>	<i>y</i>	<i>z</i>	<i>P</i>	<i>C</i>
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

$$C = x \oplus y \oplus z \oplus P$$