

Lecture 7

Combinational Logic (continue)

Outline

- ❑ Other Arithmetic Circuits
- ❑ Decoders and Encoders
- ❑ Multiplexers

Decimal Adder

- ❑ A decimal adder requires a minimum of 9 inputs and 5 outputs
 - ❑ 1 digit requires 4-bit
 - ❑ Input: 2 digits + 1-bit carry
 - ❑ Output: 1 digit + 1-bit carry
- ❑ BCD adder
 - ❑ Perform the addition of two decimal digits in BCD, together with an input carry from a previous stage
 - ❑ The output sum cannot be greater than 19 (9+9+1)

Derivation of BCD Adder

Binary Sum					BCD Sum					Decimal
K	Z ₈	Z ₄	Z ₂	Z ₁	C	S ₈	S ₄	S ₂	S ₁	
0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	1	0	0	0	0	1	1

0	1	0	1	0	1	0	0	0	0	10
0	1	0	1	1	1	0	0	0	1	11
0	1	1	0	0	1	0	0	1	0	12
0	1	1	0	1	1	0	0	1	1	13
0	1	1	1	0	1	0	1	0	0	14
0	1	1	1	1	1	0	1	0	1	15
1	0	0	0	0	1	0	1	1	0	16
1	0	0	0	1	1	0	1	1	1	17
1	0	0	1	0	1	1	0	0	0	18
1	0	0	1	1	1	1	0	0	1	19

BCD Adder

- ❑ When the binary sum is equal to or less than 1001b
 - ❑ BCD Sum = Binary Sum
 - ❑ C = 0
- ❑ When the binary sum is greater than 1001b
 - ❑ BCD Sum = Binary Sum + 0110b
 - ❑ C = 1


Z_8Z_4 Z_2Z_1	00	01	11	10
00			1	
01			1	
11			1	1
10			1	1

$$C = K + Z_8Z_4 + Z_8Z_2$$

Block Diagram of a BCD Adder

$$C = K + Z_8Z_4 + Z_8Z_2$$

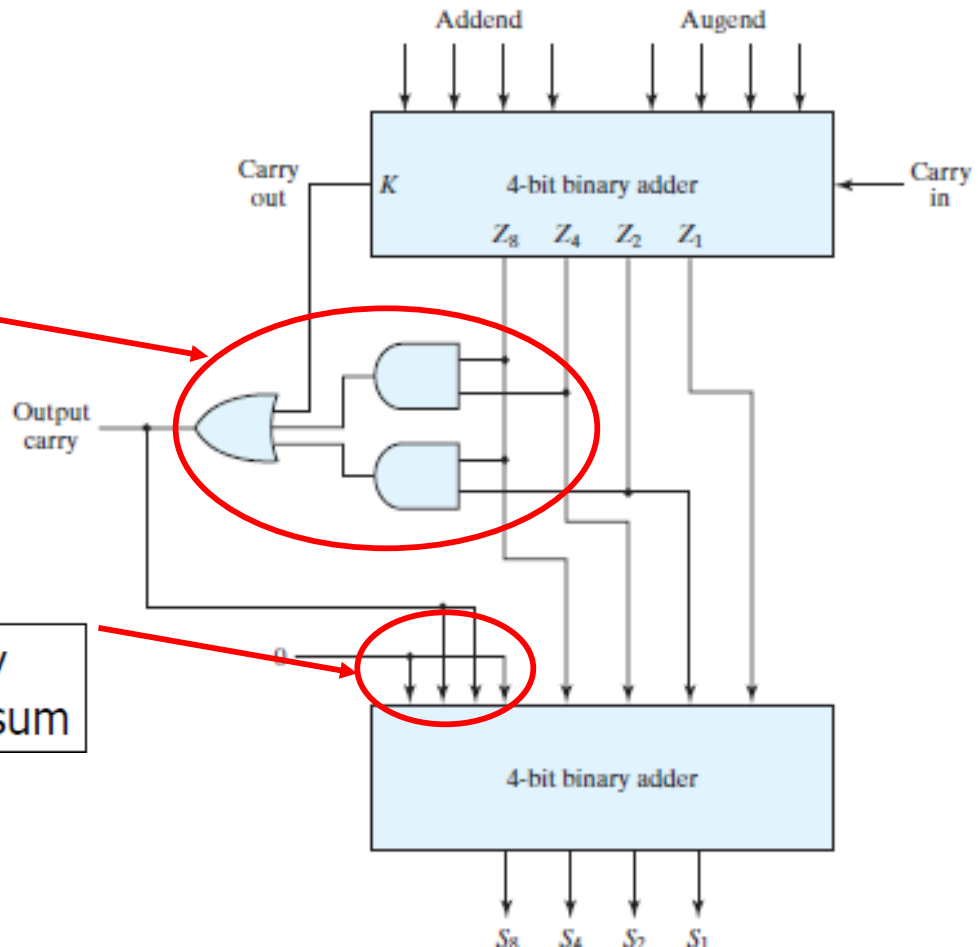
If $C = 1$, it is necessary to add 0110 to binary sum



Binary Multiplier

	B_1	B_0		
	A_1	A_0		
	<hr/>			
	A_0B_1	A_0B_0		
	A_1B_1	A_1B_0		
	<hr/>			
C_3	C_2	C_1	C_0	

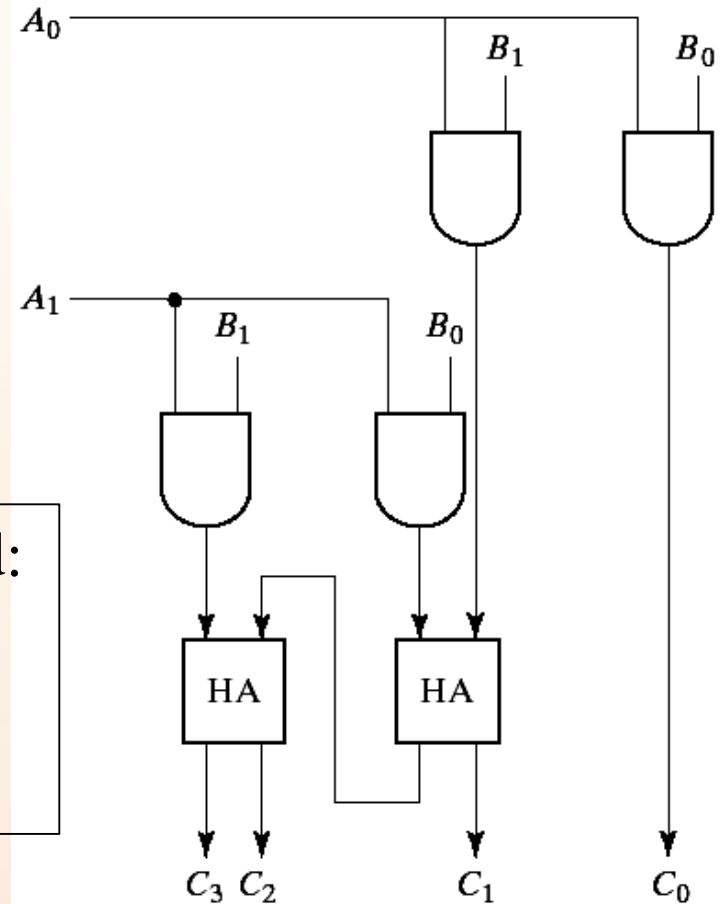For a $J \times K$ bits multiplier, we need:
($J \times K$) AND gates
($J - 1$) K-bit adders
to produce a product of $J+K$ bits




Decoder

- ❑ A circuit that converts binary information from n input lines to a maximum of 2^n unique output lines
 - ❑ May have fewer than 2^n outputs
- ❑ A n -to- m -line decoder ($m \leq 2^n$):
 - ❑ Generate the m minterms of n input variables
- ❑ For each possible input combination, there is only one output that is equal to 1
 - ❑ The output whose value is equal to 1 represents the minterm equivalent of the binary number presently available in the input lines

3-to-8-Line Decoder

 
- ❑ The 3 inputs are decoded into 8 outputs
- ❑ Each represent one of the minterms of the inputs variables



Inputs			Outputs							
x	y	z	D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

2-to-4-Line Decoder with Enable

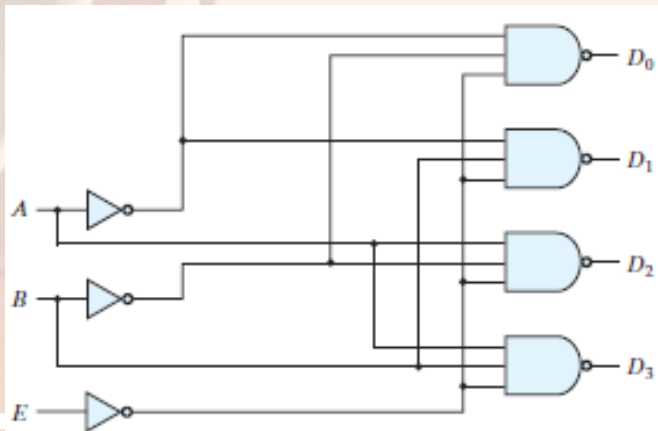
- ❑ Some decoders are constructed with NAND gates
 - ❑ Generate minterms in their complement form
- ❑ An **enable input can be added to control the operation**
 - ❑ $E=1$: disabled
 - ❑ None of the outputs are equal to 0



E	A	B	D_0	D_1	D_2	D_3
1	X	X	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0


Construct Larger Decoders

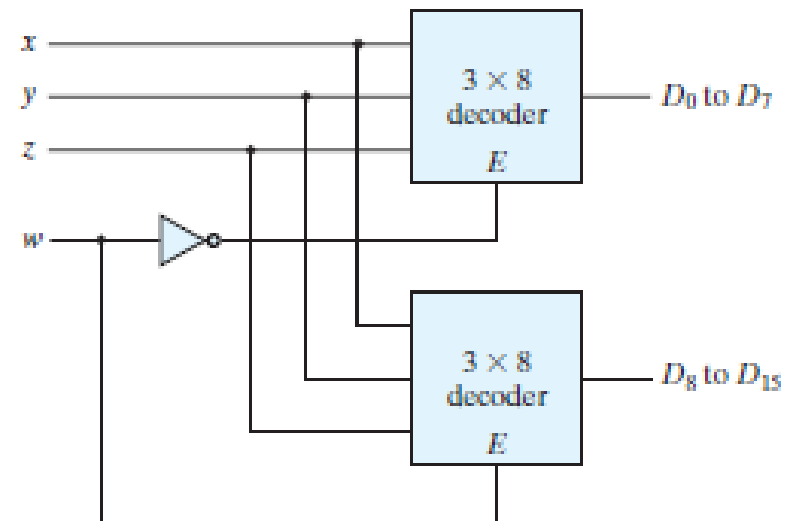- ❑ Decoders with enable inputs can be connected together to form a larger decoder
- ❑ The enable input is used as the most significant bit of the selection signal
 - ❑ $w=0$: the top decoder is enabled
 - ❑ $w=1$: the bottom one is enabled
- ❑ In general, enable inputs are a convenient feature for standard components to expand their numbers of inputs and outputs



Combinational Logic Implementation

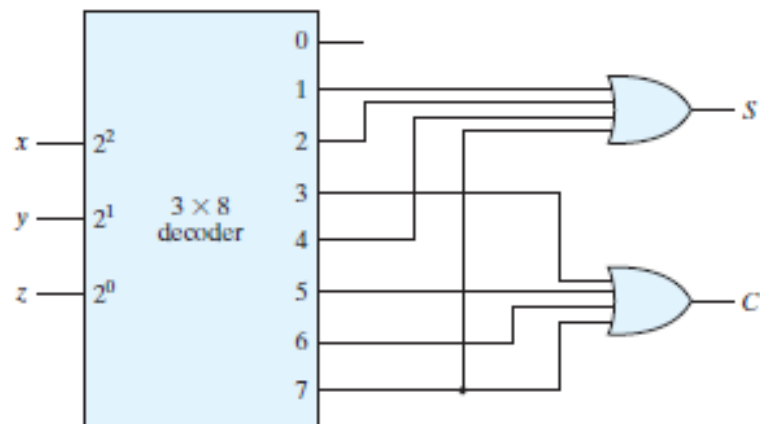- ❑ A decoder provides the 2^n minterms of n input variables
 - ❑ Can be used to form any combinational circuits with extra OR gates (sum of minterms)
- ❑ A function having a list of k minterms can be expressed in its complemented form F' with $2^n - k$ minterms
 - ❑ If $k > 2^n/2$, F' will have fewer minterms (fewer OR gates)
 - ❑ NOR gates are used instead for implementing F'



$$S(x,y,z) = \Sigma (1,2,4,7)$$

$$C(x,y,z) = \Sigma (3,5,6,7)$$

Encoder



- ❑ A circuit that performs the inverse operation of a decoder
 - ❑ Have 2^n (or fewer) input lines and n output lines
 - ❑ The output lines generate the binary code of the input positions
- ❑ Only one input can be active at any given time
- ❑ An extra output may be required to distinguish the cases that $D_0 = 1$ and all inputs are 0

Inputs								Outputs		
D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7	x	y	z
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

$$\begin{aligned}z &= D_1 + D_3 + D_5 + D_7 \\y &= D_2 + D_3 + D_6 + D_7 \\x &= D_4 + D_5 + D_6 + D_7\end{aligned}$$

Multiplexer

  - ❑ circuit that selects binary information from one of many input lines and directs it to a single output lines
 - ❑ Have 2^n input lines and n selection lines
 - ❑ Act like an electronic switch (also called a **data selector**)
- ❑ For the following 2-to-1-line multiplexer:
 - ❑ $S=0 \rightarrow Y = I_0$; $S=1 \rightarrow Y = I_1$




VHDL code for a 2-to-1 multiplexer.

```
LIBRARY ieee ;
USE ieee.std logic 1164.all ;
ENTITY mux2to1 IS
PORT ( w0, w1, s : IN STD LOGIC ;
      f : OUT STD LOGIC ) ;
END mux2to1 ;
ARCHITECTURE Behavior OF mux2to1 IS
BEGIN
WITH s SELECT
    f <w0 WHEN '0',
    w1 WHEN OTHERS ;
END Behavior ;
```

Quadruple 2-to-1-Line Multiplexer

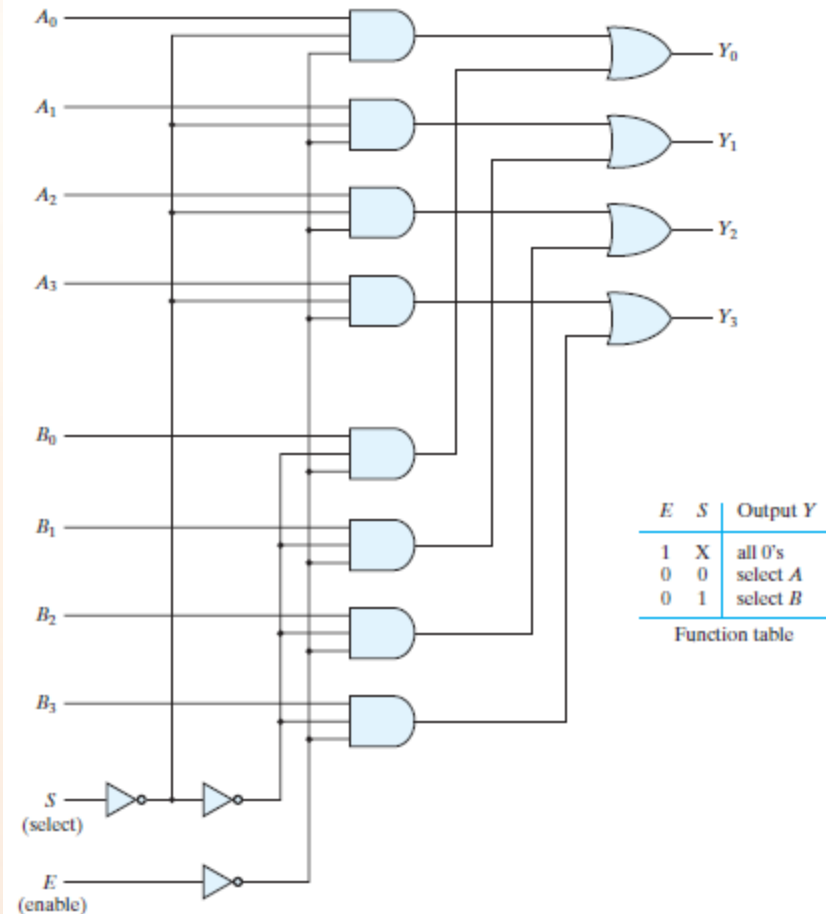- ❑ Multiplexers can be combined with **common selection inputs to provide multiple-bit** selection logic
- ❑ Quadruple 2-to-1-line multiplexer:
- ❑ Four 2-to-1-line multiplexers
 - ❑ Each capable of selecting one bit of the 2 4-bit inputs
 - ❑ E: enable input
 - ❑ E=1: disable the circuit (all outputs are 0)




Boolean Function Implementation

- ❑ A multiplexer is essentially a decoder with an external OR gate
 - ❑ Can be used to implement Boolean functions without extra logic
- ❑ To implement a Boolean function of n variables:
 - ❑ Use a multiplexer with $n - 1$ selection inputs
 - ❑ The first $n - 1$ variables are connected to the selection inputs
 - ❑ The remaining variable is used for the data inputs

$$F(x,y,z) = \Sigma(1,2,6,7)$$

x	y	z	F	
0	0	0	0	$F = z$
0	0	1	1	
0	1	0	1	$F = z'$
0	1	1	0	
1	0	0	0	$F = 0$
1	0	1	0	
1	1	0	1	$F = 1$
1	1	1	1	

(a) Truth table

 


(b) Multiplexer implementation

Implementing a 4-Input Function

$$F(A,B,C,D) = \Sigma(1,3,4,11,12,13,14,15)$$

<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>F</i>	
0	0	0	0	0	
0	0	0	1	1	$F = D$
0	0	1	0	0	
0	0	1	1	1	$F = D$
0	1	0	0	1	$F = D'$
0	1	0	1	0	
0	1	1	0	0	
0	1	1	1	0	$F = 0$
1	0	0	0	0	
1	0	0	1	0	$F = 0$
1	0	1	0	0	
1	0	1	1	1	$F = D$
1	1	0	0	1	
1	1	0	1	1	$F = 1$
1	1	1	0	1	
1	1	1	1	1	$F = 1$

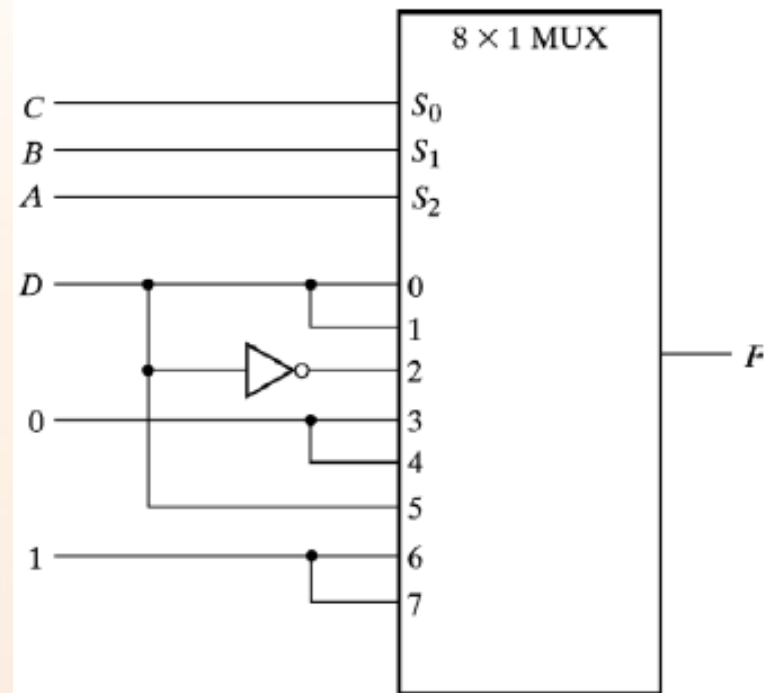

Three-State Gate

- ❑ A circuit that exhibits three states
 - ❑ logic 1, logic 0, and **high-impedance (z)**
- ❑ The high-impedance state acts like an open circuit (disconnected)
- ❑ The most commonly used three-state gate is the buffer gate
 - ❑ $C=0 \rightarrow$ disabled (high-impedance) ; $C=1 \rightarrow$ enabled (pass)
 - ❑ Can be used at the output of a function without altering the internal implementation

