

Lecture 7

Synchronous Sequential Logic

Outline

- ❑ Sequential Circuits
- ❑ Latches
- ❑ Flip-Flops

Sequential Circuits

- ❑ Consist of a combinational circuit to which storage elements are connected to form a feedback path
- ❑ State . the state of the memory devices now, also called **current state**
- ❑ Next states and outputs are functions of inputs and present states of storage elements


 


Fig. 5-1 Block Diagram of Sequential Circuit

Two Types of Sequential Circuits

- ❑ Asynchronous sequential circuit
 - ❑ Depends upon the input signals at **any instant of time and** their change order
 - ❑ May have better performance but hard to design

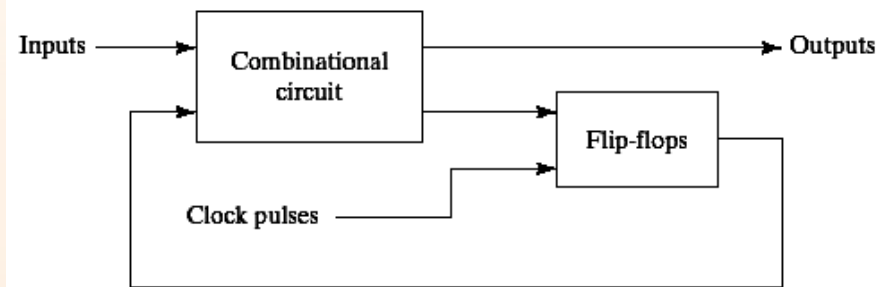- ❑ Synchronous sequential circuit
 - ❑ Defined from the knowledge of its signals at **discrete instants of time**
 - ❑ Much easier to design (preferred design style)
 - ❑ Synchronized by a periodic train of clock pulses



(a) Block diagram



(b) Timing diagram of clock pulses

Memory Elements


- ❑ Allow sequential logic design
- ❑ Latch . a level-sensitive memory element
 - ❑ SR latches
 - ❑ D latches
- ❑ Flip-Flop . an edge-triggered memory element
 - ❑ Master-slave flip-flop
 - ❑ Edge-triggered flip-flop
- ❑ RAM and ROM . a mass memory element

Latches

- ❑ The most basic types of flip-flops operate with signal levels
- ❑ The basic circuits from which all flip-flops are constructed
- ❑ Useful for storing binary information and for the design of asynchronous sequential circuits
 - ❑ Not practical for use in synchronous sequential circuits
 - ❑ Avoid to use latches as possible in synchronous sequential circuits to avoid design problems

SR Latch

 - ❑ A circuit with two cross-coupled NOR gates or two cross-coupled NAND gates
- ❑ Two useful states:
 - ❑ $S=1, R=0$ " set state (Q will become to 1)
 - ❑ $S=0, R=1$ " reset state (Q will become to 0)
- ❑ When $S=0$ and $R=0$ " keep the current value




(a) Logic diagram

S	R	Q	Q'	
1	0	1	0	
0	0	1	0	(after $S = 1, R = 0$)
0	1	0	1	
0	0	0	1	(after $S = 0, R = 1$)
1	1	0	0	

(b) Function table

Undefined State in SR Latch

 

(a) Logic diagram

S	R	Q	\bar{Q}	
1	0	1	0	Set state
0	0	1	0	
0	1	0	1	Reset state
0	0	0	1	
1	1	0	0	Undefined

(b) Function table

Should be very careful for this case

SR Latch with NAND Gates

- The SR latches constructed with two cross-coupled NAND gates are **active-low**
 - $S=1, R=0$ " reset state (Q will become to 0)
 - $S=0, R=1$ " set state (Q will become to 1)
 - $S=1, R=1$ " unchanged


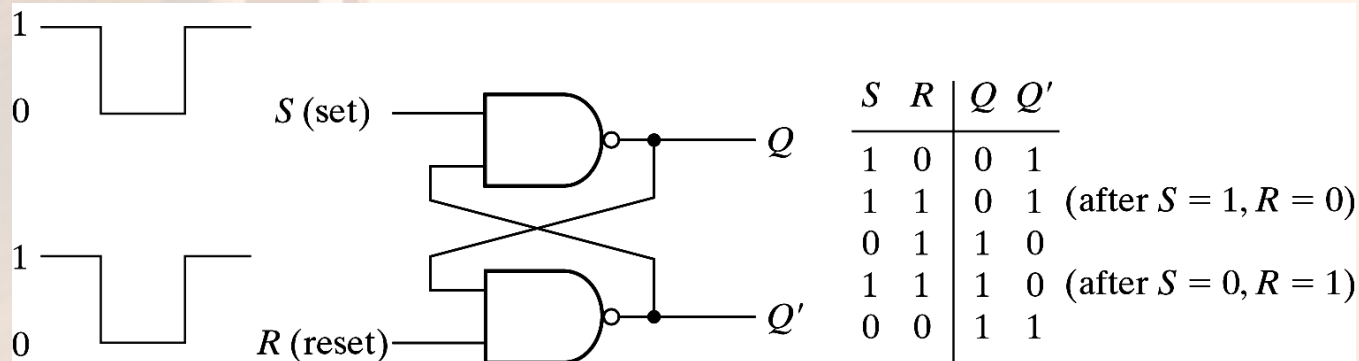


Fig. 5-4 SR Latch with NAND Gates

SR Latch with Control Input

 - ❑ Add an additional control input to determine when the state of the latch can be changed
- ❑ $C=0$: S and R are disabled (no change at outputs)
- ❑ $C=1$: S and R are active-high



(a) Logic diagram


C	S	R	Next state of Q
0	X	X	No change
1	0	0	No change
1	0	1	$Q = 0$; Reset state
1	1	0	$Q = 1$; set state
1	1	1	Indeterminate

(b) Function table

Fig. 5-5 SR Latch with Control Input

D Latch

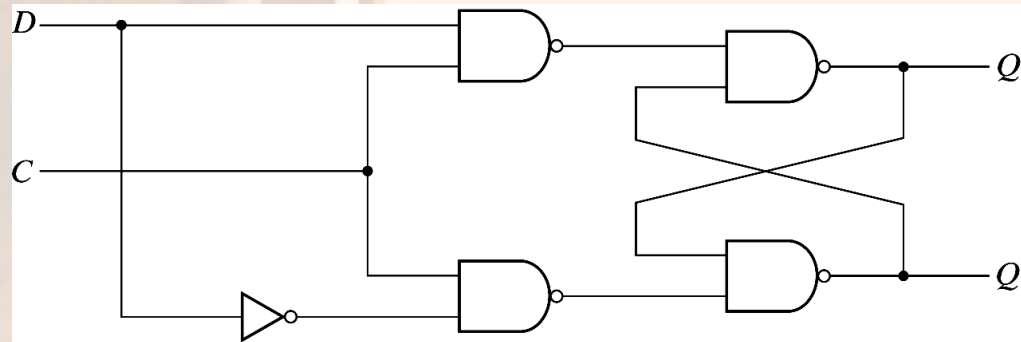- D latch has only two inputs: D(data) and C(control)
 - Use the value of D to set the output value
 - Eliminate the indeterminate state in the SR latches
- The D input goes directly to the S input and its complement is applied to the R input
 - $D=1 \rightarrow Q=1 \rightarrow S=1, R=0$



(a) Logic diagram

C	D	Next state of Q
0	X	No change
1	0	$Q = 0$; Reset state
1	1	$Q = 1$; Set state

(b) Function table

Fig. 5-6 D Latch

Graphic Symbols for Latches

 


Fig. 5-7 Graphic Symbols for Latches

Flip-Flops

- ❑ The state of a latch or flip-flop is switched by a change in the control input
- ❑ This momentary change is called a **trigger**
- ❑ Latch: level-sensitive
- ❑ Flip-Flop: edge-triggered

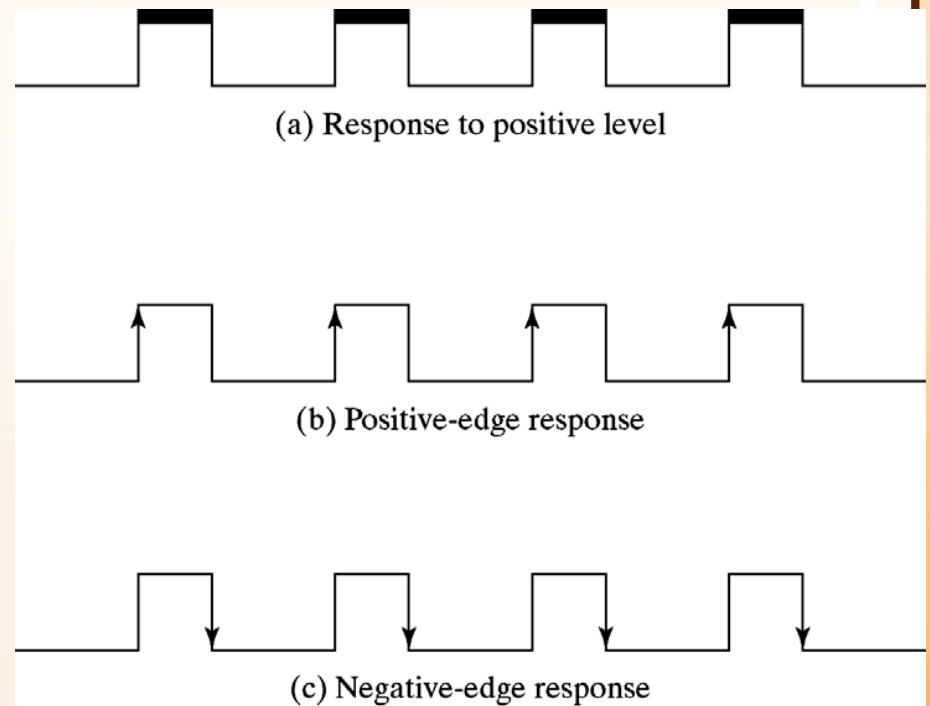


Fig. 5-8 Clock Response in Latch and Flip-Flop


Latch vs. Flip-Flop

❑ Latch:

- ❑ Change stored value under specific status of the control signals
- ❑ Transparent for input signals when control signal is .on.
- ❑ May cause combinational feedback loop and extra changes at the output

❑ Flip-Flop:

 - ❑ Can only change stored value by a momentary switch in value of the control signals
- ❑ Cannot .see. the change of its output in the same clock pulse
- ❑ Encounter fewer problems than using latches



reading

- M. Morris Mano , Michael D. Ciletti “Digital Design With an Introduction to the Verilog HDL” FIFTH EDITION
 - Sections: 5.1 to 5.4