


Lecture 8

Synchronous Sequential Logic continue

Outline

- ❑ Flip Flops
- ❑ Analysis of Clocked Sequential Circuits
- ❑ Design Procedure

Master-Slave D Flip-Flop

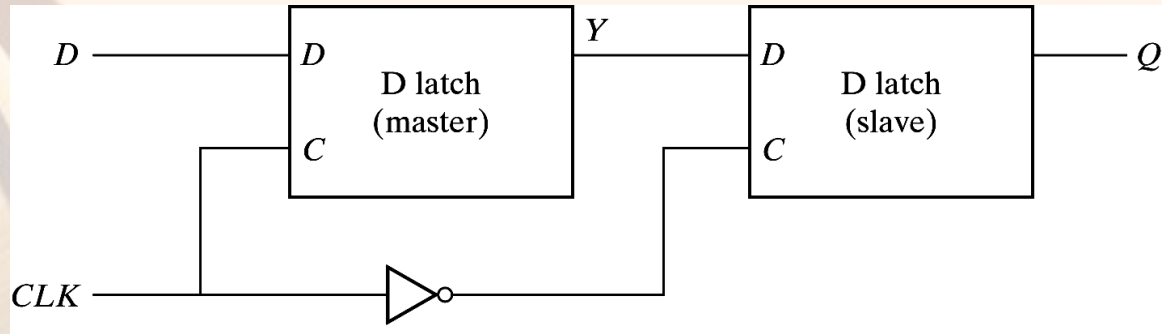

- ❑ Constructed with two D latches and an inverter
- ❑ The first latch (master) is enabled when $CLK=1$
 - ❑ It reads the input changes but stops before the second one
- ❑ The second latch (slave) is enabled when $CLK=0$
 - ❑ Close the first latch to isolate the input changes
 - ❑ Deliver the final value at the moment just before CLK changes
- ❑ The circuit samples the D input and changes its output Q only at the **negative-edge of the controlling clock**

Edge-Triggered D Flip-Flop

- ❑ If only SR latches are available, three latches are required
- ❑ Two latches are used for locking the two inputs (CLK & D)
- ❑ The final latch provides the output of the flip-flop


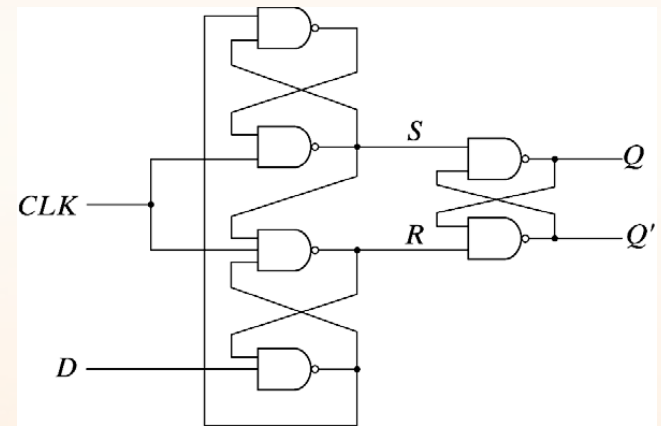


Fig. 5-10 *D*-Type Positive-Edge-Triggered Flip-Flop

 

Graphic symbol for edge-triggered *D* flip-flop

Setup & Hold Times


- ❑ The response time of a flip-flop to input changes must be taken into consideration
- ❑ Setup Time: The length of time that data must stabilize before the clock transition
 - ❑ The maximum data path is used to determine if the setup time is met
- ❑ Hold Time: The length of time that data must remain stable at the input pin after the active clock transition
 - ❑ The minimum data path is used to determine if hold time is met

Other Flip-Flops


- ❑ The most economical and efficient flip-flop is the edge-triggered D flip-flop
 - ❑ It requires the smallest number of gates
- ❑ Other types of flip-flops can be constructed by using the D flip-flop and external logic
 - ❑ JK flip-flop
 - ❑ T flip-flops
- ❑ Three major operations that can be performed with a flip-flop:
 - ❑ Set it to 1
 - ❑ Reset it to 0
 - ❑ Complement its output

Edge-Triggered JK Flip-Flop

$$D = JQ' + K'Q$$

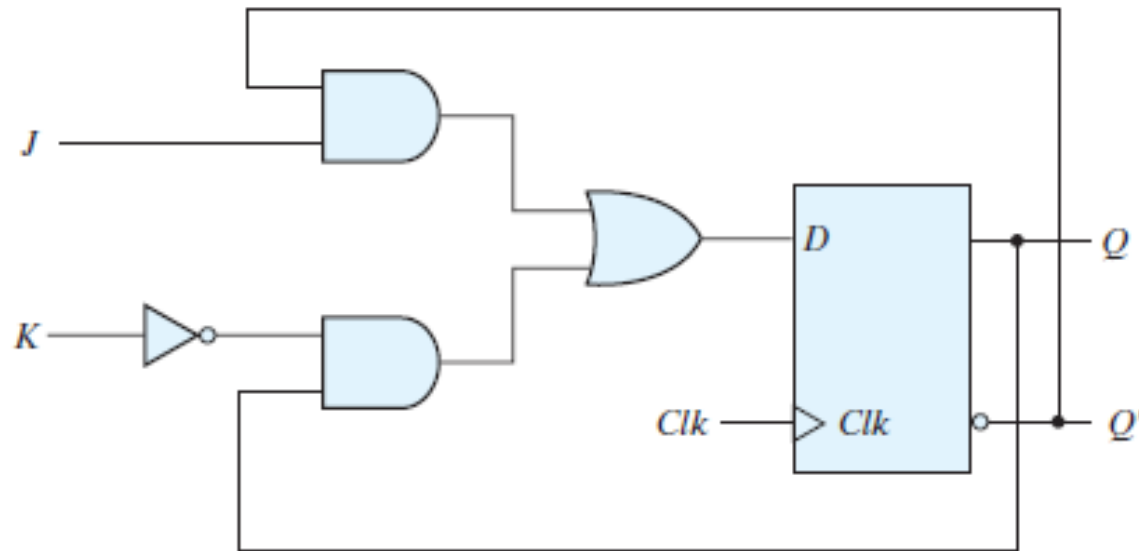

(a) Circuit diagram

 

(b) Graphic symbol

FIGURE 5.12: JK flip-flop

Edge-Triggered T Flip-Flop

$$D = T \oplus Q = TQ' + T'Q$$

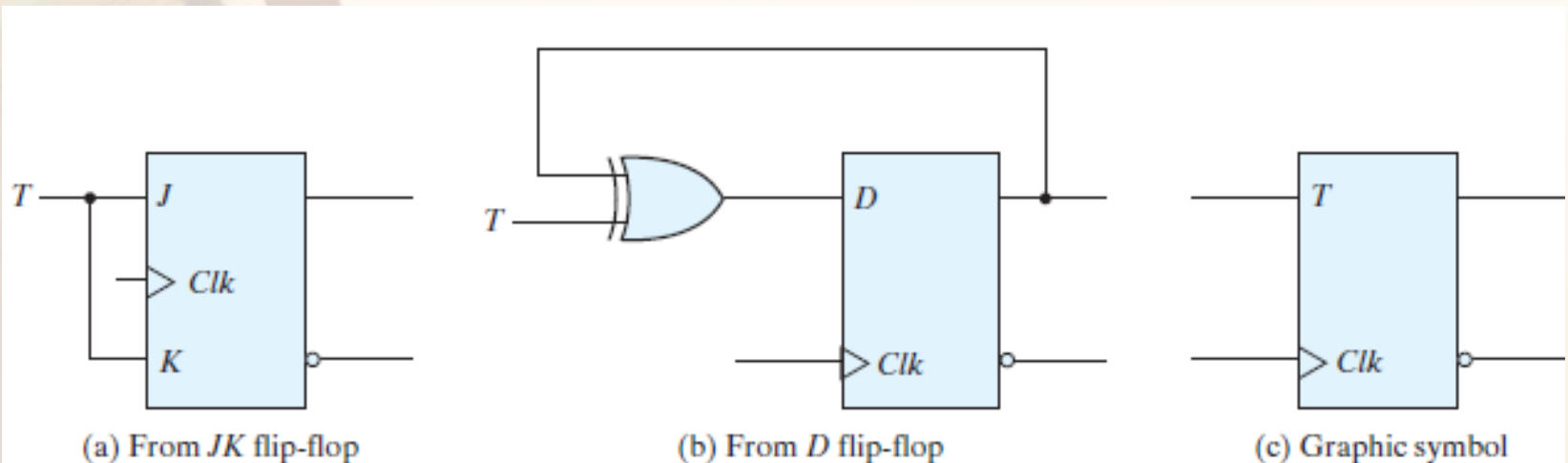


FIGURE 5.13: T flip-flop

T=0: hold
T=1: toggle

Characteristic Tables

- Define the logical properties in tabular form

D Flip-Flop

D	Q(t + 1)	
0	0	Reset
1	1	Set

JK Flip-Flop

J	K	Q(t + 1)	
0	0	$Q(t)$	No change
0	1	0	Reset
1	0	1	Set
1	1	$Q'(t)$	Complement

T Flip-Flop

T	Q(t + 1)	
0	$Q(t)$	No change
1	$Q'(t)$	Complement

Characteristic Equations

- ❑ Algebraically describe the next state
- ❑ Can be derived from characteristic tables

- ❑ D flip-flop:

$$Q(t + 1) = D$$

- ❑ JK flip-flop:


$$Q(t + 1) = JQ' + K'Q$$

- ❑ T flip-flop:

$$Q(t + 1) = T \oplus Q = TQ' + T'Q$$

Direct Inputs

- ❑ Force the flip-flop to a particular state immediately
 - ❑ Independent of clock signal
 - ❑ Have higher priority than any other inputs
 - ❑ Useful to bring all flip-flops from unknown into known state while power up
- ❑ The input that sets the flip-flop to 1 is called **preset or direct set**
- ❑ The input that clears the flip-flop to 0 is called **clear or direct reset**
- ❑ Also called **asynchronous set/reset**

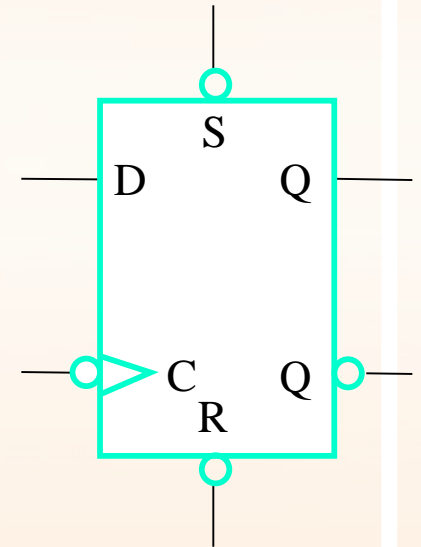

Sequential Circuit Analysis

- ❑ The behavior of a clocked sequential circuit is determined from
 - ❑ The inputs
 - ❑ The outputs
 - ❑ The state of its flip-flops
- ❑ The outputs and the next state are both a function of the inputs and the present state
- ❑ To analyze a sequential circuit, we can use
 - ❑ State equations
 - ❑ State table
 - ❑ State diagram
 - ❑ Flip-Flop input equations

State Equations


- ❑ Input: $x(t)$
- ❑ Output: $y(t)$
- ❑ State: $(A(t), B(t))$
- ❑ What is the Output Function?

$$y(t) = \bar{x}(t)(B(t) + A(t))$$

- ❑ What is the Next State Function?

$$A(t+1) = A(t)x(t) + B(t)x(t)$$

$$B(t+1) = \bar{A}(t)x(t)$$

 

State Table(transition table)

- ❑ Enumerate the time sequence of inputs, outputs, and flip-flop states
 - ❑ Also called transition table
 - ❑ Similar to list the truth table of state equations
- ❑ Consist of four sections
 - ❑ Present state, input, next state, and output
- ❑ A sequential circuit with m flip-flops and n inputs need 2^{m+n} rows in the state table

Present state		input	Next state		output
A	B	x	A	B	y
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0

Second Form of State Table

- ❑ The state table has only three section: present state, next state, and output
- ❑ The input conditions are enumerated under next state and output sections

Present State A(t) B(t)	Next State		Output	
	x(t)=0 A(t+1)B(t+1)	x(t)=1 A(t+1)B(t+1)	x(t)=0 y(t)	x(t)=1 y(t)
0 0	0 0	0 1	0	0
0 1	0 0	1 1	1	0
1 0	0 0	1 0	1	0
1 1	0 0	1 0	1	0

State Diagram

- ❑ Graphically represent the information in a state table
 - ❑ Circle: a state (with its state value inside)
 - ❑ Directed lines: state transitions (with inputs/outputs above)
- ❑ Ex: starting from state 00
 - ❑ If the input is 0, it stays at state 00 with output=0
 - ❑ If the input is 1, it goes to state 01 with output=0
- ❑ The state table is easier to derive from a given logic diagram and state equations
- ❑ The state diagram is suitable for human interpretation

 


FIGURE 5.16
State diagram of the circuit of Fig. 5.15

Flip-Flop Input Equations

- ❑ To draw the logic diagram of a sequential circuit, we need
 - ❑ The type of flip-flops
 - ❑ A list of Boolean expressions of the combinational circuits
- ❑ The Boolean functions for the circuit that generates external outputs is called output equations
- ❑ The Boolean functions for the circuit that generates the inputs to flip-flops is flip-flop input equations
- ❑ Sometimes called excitation equations
- ❑ The flip-flop input equations provide a convenient form for specifying the logic diagram of a sequential circuit
- ❑ Ex: (Fig. 5-15)


Input:	Output:
$DA = Ax + Bx$	$y = (A + B)x'$
$DB = A'x$	

Design Procedure

- ❑ Design procedure of synchronous sequential circuits:
 1. Derive a state diagram for the circuit from specifications
 2. Reduce the number of states if necessary
 3. Assign binary values to the states
 4. Obtain the binary-coded state table
 5. Choose the type of flip-flop to be used
 6. Derive the simplified flip-flop input equations and output equations
 7. Draw the logic diagram
- ❑ Step 4 to 7 can be automated
 - ❑ Use HDL synthesis tools

Synthesis Using D Flip-Flops

 - Ex: design a circuit that detects a sequence of three or more consecutive 1's in a string of bits coming through an input line



$$A(t+1) = D_A(A, B, x) = \sum (3, 5, 7)$$

$$B(t+1) = D_B(A, B, x) = \sum (1, 5, 7)$$

$$y(A, B, x) = \sum (6, 7)$$

Present state		Input	Next state		Output
A	B	X	A	B	y
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	1	0	0
1	0	0	0	0	0
1	0	1	1	1	0
1	1	0	0	0	1
1	1	1	1	1	1

Synthesis Using D Flip-Flops

 
 
 
 


Fig. 5-26 Logic Diagram of Sequence Detector

Excitation Tables

- ❑ Record the flip-flop input conditions that will cause the required transition in STG
 - ❑ Equal to next state equations for D flip-flop
- ❑ For JK flip-flop:
 - ❑ $J=0, K=X$: no change ($JK=00$) or set to zero ($JK=01$)
 - ❑ $J=1, K=X$: toggle ($JK=11$) or set to one ($JK=10$)
 - ❑ $J=X, K=1$: toggle ($JK=11$) or set to zero ($JK=01$)
 - ❑ $J=X, K=0$: no change ($JK=00$) or set to one ($JK=10$)

JK F/F	Q(t)	Q(t+1)	J	K
	0	0	0	X
	0	1	1	X
	1	0	X	1
	1	1	X	0

Q(t)	Q(t+1)	T	T F/F
0	0	0	
0	1	1	
1	0	1	
1	1	0	

Synthesis Using JK Flip-Flops

- Derive the state table with the excitation inputs

Present State		Input X	Next State		Flip-Flop Inputs			
A	B		A	B	J _A	K _A	J _B	K _B
0	0	0	0	0	0	X	0	X
0	0	1	0	1	0	X	1	X
0	1	0	1	0	1	X	X	1
0	1	1	0	1	0	X	X	0
1	0	0	1	0	X	0	0	X
1	0	1	1	1	X	0	1	X
1	1	0	1	1	X	0	X	0
1	1	1	0	0	X	1	X	1


Synthesis Using JK Flip-Flops

		B			
		Bx	00	01	11
A	0	m_0	m_1	m_3	m_2 1
	1	m_4 X	m_5 X	m_7 X	m_6 X
		x			
		$J_A = Bx'$			

		B			
		Bx	00	01	11
A	0	m_0 X	m_1 X	m_3 X	m_2 X
	1	m_4	m_5	m_7 1	m_6
		x			
		$K_A = Bx$			


		B			
		Bx	00	01	11
A	0	m_0	m_1 1	m_3 X	m_2 X
	1	m_4	m_5 1	m_7 X	m_6 X
		x			
		$J_B = x$			

		B			
		Bx	00	01	11
A	0	m_0 X	m_1 X	m_3	m_2 1
	1	m_4 X	m_5 X	m_7 1	m_6
		x			
		$K_B = (A \oplus x)'$			

 

Synthesis using T Flip-Flop

- 3-bit binary counter

 

Present State			Next State			Flip-Flop Inputs		
A2	A1	A0	A2	A1	A0	T _{A2}	T _{A1}	T _{A0}
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	0	1
1	1	1	0	0	0	1	1	1

T flip-Flop for 3-bit binary counter


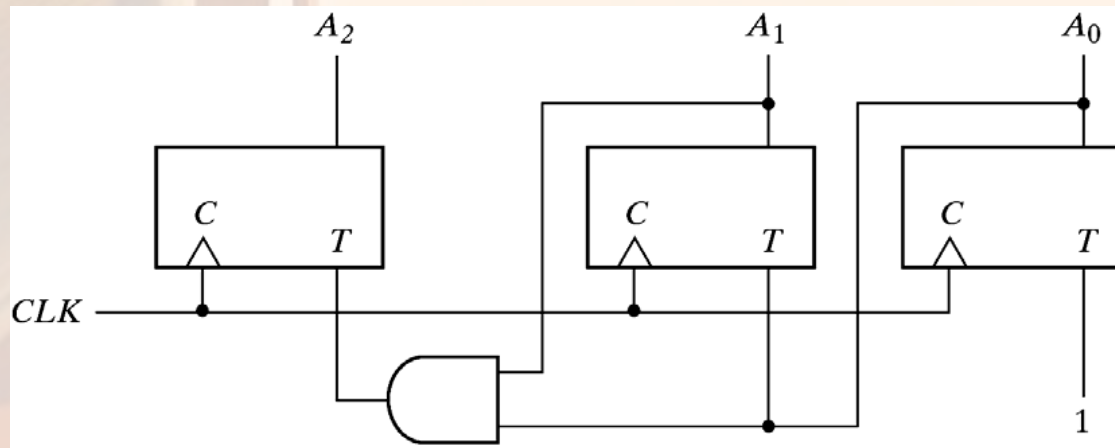
 


FIGURE 5.34: Logic diagram of three-bit binary counter

Home work 1

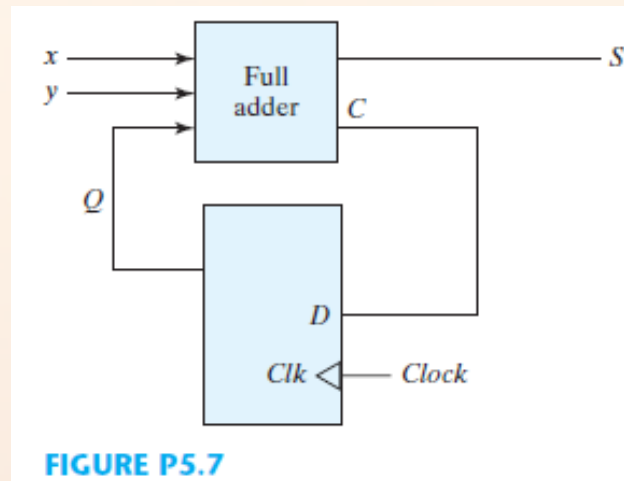- A sequential circuit has one flip-flop Q , two inputs x and y , and one output S . It consists of a full-adder circuit connected to a D flip-flop, as shown in Fig. P5.7. Derive the state table and state diagram of the sequential circuit.



Home work 2

Design a sequential circuit with two *D flip-flops A and B*, and one input x . When $x = 0$, the state of the circuit remains the same. When $x = 1$, the circuit goes through the state transitions from 00 to 01, to 11, to 10, back to 00, and repeats.

Home work 3

Design a sequential circuit with two *JK flip-flops A and B* and two inputs *E and F*. If $E = 0$, the circuit remains in the same state regardless of the value of F . When $E = 1$ and $F = 1$, the circuit goes through the state transitions from 00 to 01, to 10, to 11, back to 00, and repeats. When $E = 1$ and $F = 0$, the circuit goes through the state transitions from 00 to 11, to 10, to 01, back to 00, and repeats

reading

- M. Morris Mano , Michael D. Ciletti "Digital Design With an Introduction to the Verilog HDL" FIFTH EDITION
 - Sections: 5.4 ,5.5(pages 198-214)