

# Lecture 9

## Registers and Counters

# Outline

- Registers
- Shift Registers
- Ripple Counters
- Synchronous Counters
- Random-Access Memory

# Registers and Counters

## ❑ Register:


- ❑ A set of flip-flops, possibly with added combinational gates, that perform data-processing tasks
- ❑ Store and manipulate information in a digital system

## ❑ Counter:

- ❑ A register that goes through a predetermined sequence of states
- ❑ A special type of register
- ❑ Employed in circuits to sequence and control operations

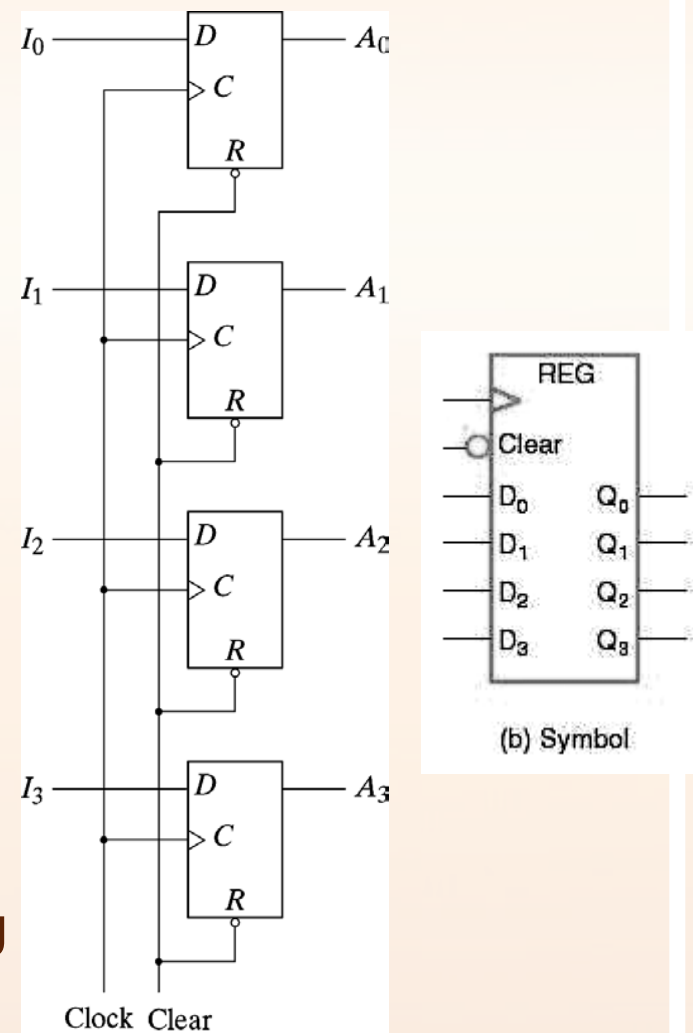
# The Simplest Register

- ❑ Consist of only flip-flops
- ❑ Triggered by common clock input
- ❑ The Clear input goes to the R (reset) input of all flip-flops
  - ❑ Clear = 0 " all flip-flops are reset **asynchronously**
- ❑ The Clear input is useful for cleaning the registers to all 0's prior to its clocked operation
  - ❑ Must maintain at logic 1 during normal operations


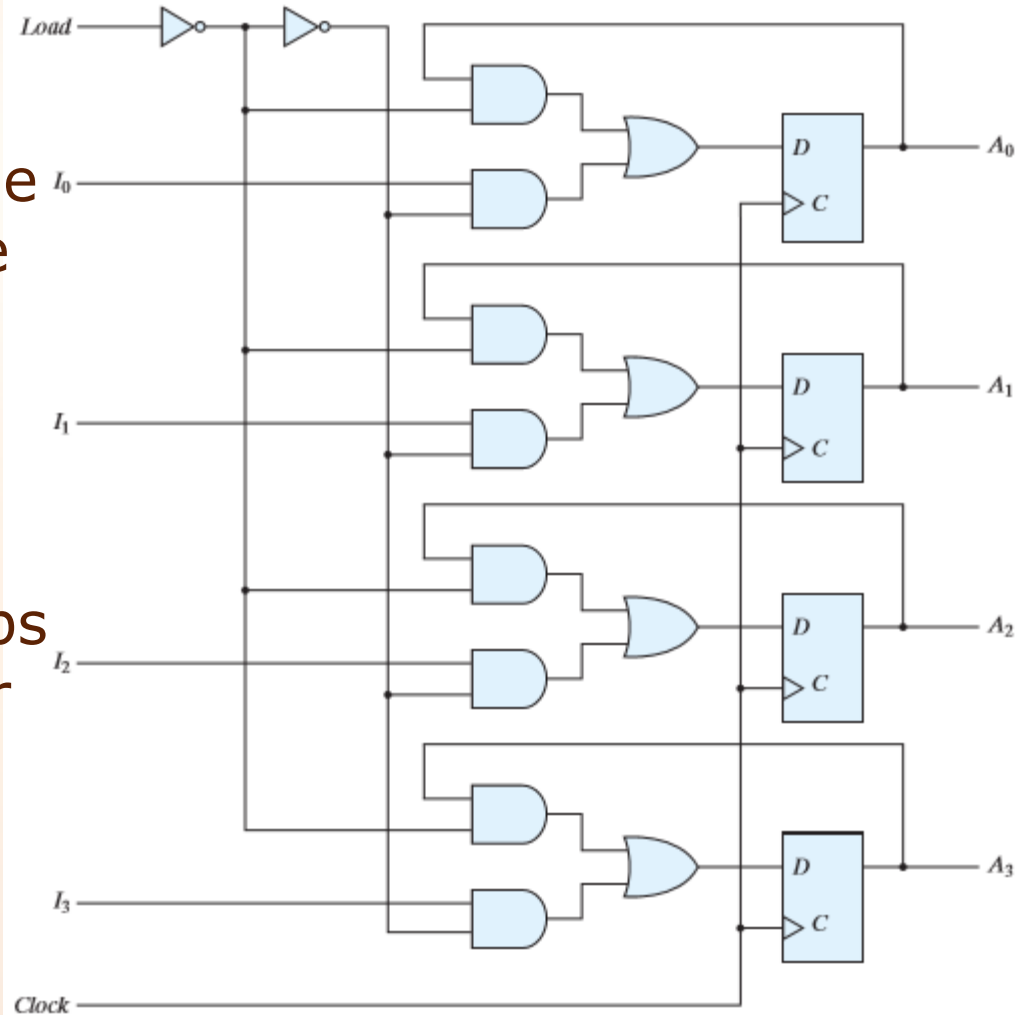
# Register with Parallel Load

- When Load = 1, all the bits of data inputs are transferred into the registers
  - Parallel loaded
- When Load = 0, the outputs of the flip-flops are connected to their respective inputs
  - Keep no change



# The Simplest Shift Register

- ❑ Shift register: a register capable of shifting its binary information in one or both directions
- ❑ The simplest form: consist of only a chain of flip-flops in cascade


 


Fig. 6-3 4-Bit Shift Register

# Binary Ripple Counter

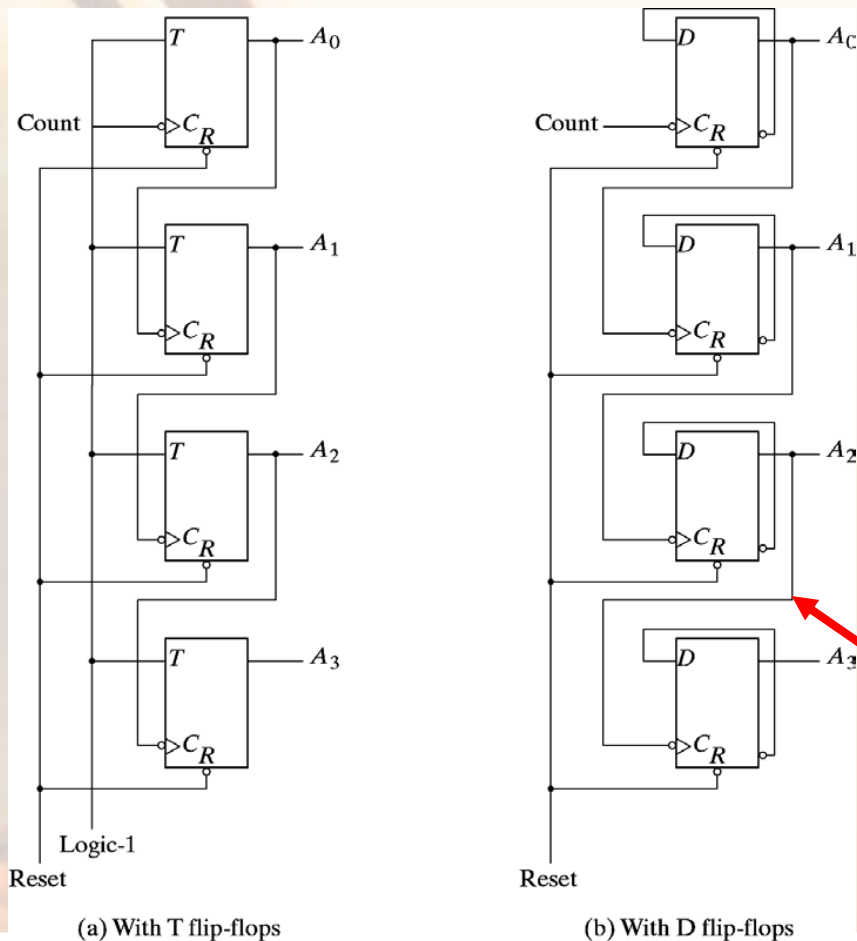

## Binary Count Sequence

A <sub>3</sub>	A <sub>2</sub>	A <sub>1</sub>	A <sub>0</sub>
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0

the output transition triggers the next flip-flop

# BCD Ripple Counter

- ❑ The count will return to 0 after 9
- ❑ Q1: always complemented
- ❑ Q2: inverted when Q8 = 0 and Q1 = 1 → 0
- ❑ Q4: inverted when Q2 = 1 → 0
- ❑ Q8: when Q1 = 1 → 0
- ❑ if (Q2 = Q4 = 1) Q8 is inverted
- ❑ else Q8 = 0


 


Fig. 6-9 State Diagram of a Decimal BCD-Counter

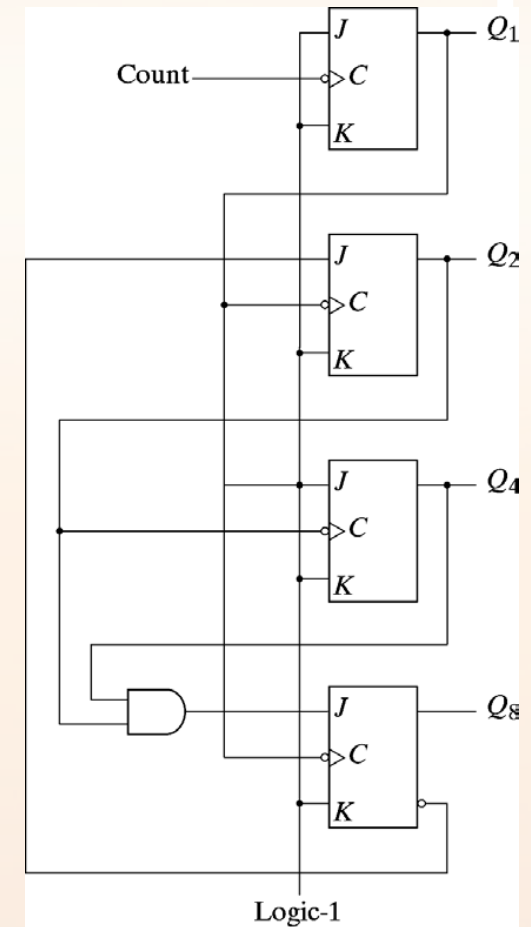



# Ripple v.s. Synchronous

- ❑ Ripple counters:
  - ❑ Flip-flops are triggered by the outputs of another flip-flops
  - ❑ Triggering source may not the same for each flip-flop
  - ❑ The flip-flops are changed serially
- ❑ Synchronous counters:
  - ❑ Flip-flops are triggered by common clock pulses
  - ❑ Triggering sources are the same for all flip-flops
  - ❑ All operations are performed simultaneously

# Design a BCD Counter

□ Go through normal sequential circuit design procedure

Present State				Next State				Output	Flip-Flop Inputs			
Q <sub>8</sub>	Q <sub>4</sub>	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>8</sub>	Q <sub>4</sub>	Q <sub>2</sub>	Q <sub>1</sub>	y	TQ <sub>8</sub>	TQ <sub>4</sub>	TQ <sub>2</sub>	TQ <sub>1</sub>
0	0	0	0	0	0	0	1	0	0	0	0	1
0	0	0	1	0	0	1	0	0	0	0	1	1
0	0	1	0	0	0	1	1	0	0	0	0	1
0	0	1	1	0	1	0	0	0	0	1	1	1
0	1	0	0	0	1	0	1	0	0	0	0	1
0	1	0	1	0	1	1	0	0	0	0	1	1
0	1	1	0	0	1	1	1	0	0	0	0	1
0	1	1	1	1	0	0	0	0	1	1	1	1
1	0	0	0	1	0	0	1	0	0	0	0	1
1	0	0	1	0	0	0	0	1	1	0	0	1

$$TQ_1 = 1$$

$$TQ_2 = Q_8'Q_1$$




$$TQ_4 = Q_2Q_1$$

$$TQ_8 = Q_8Q_1 + Q_4Q_2Q_1$$

$$y = Q_8Q_1$$

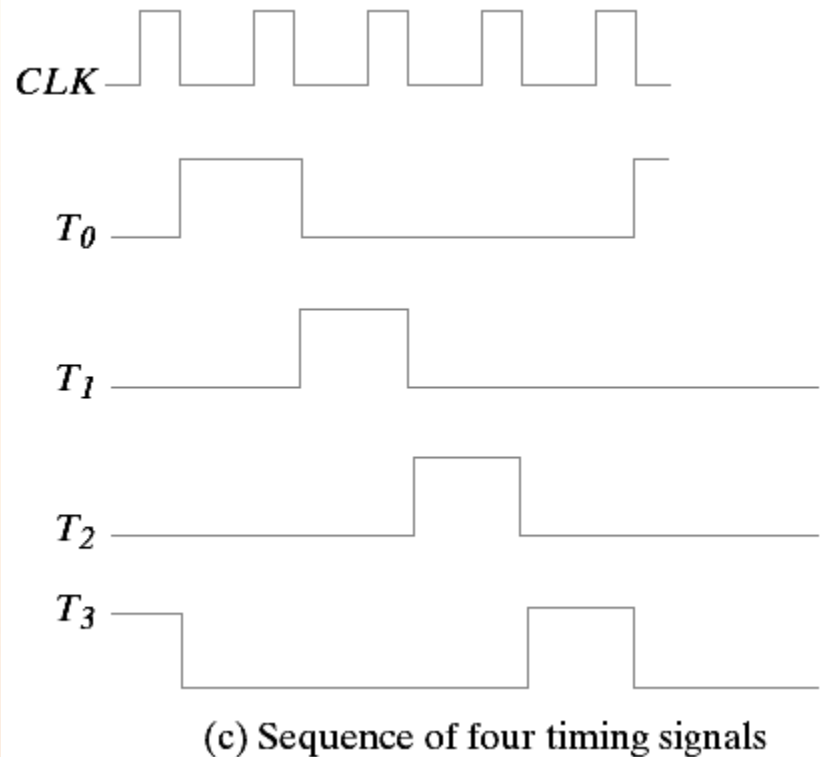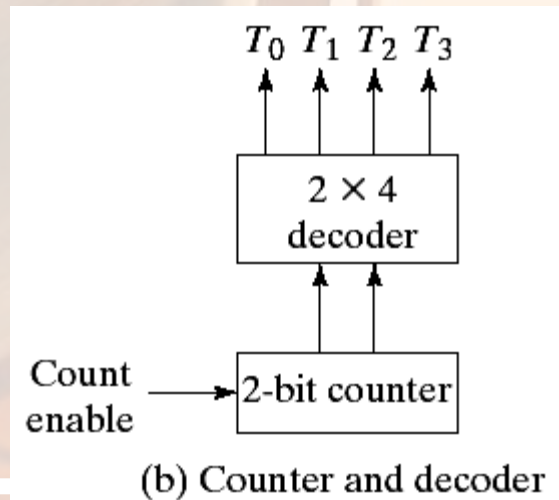 
# Ring Counter

Ring counter: a circular shift register with only one flip-flop being set at any time


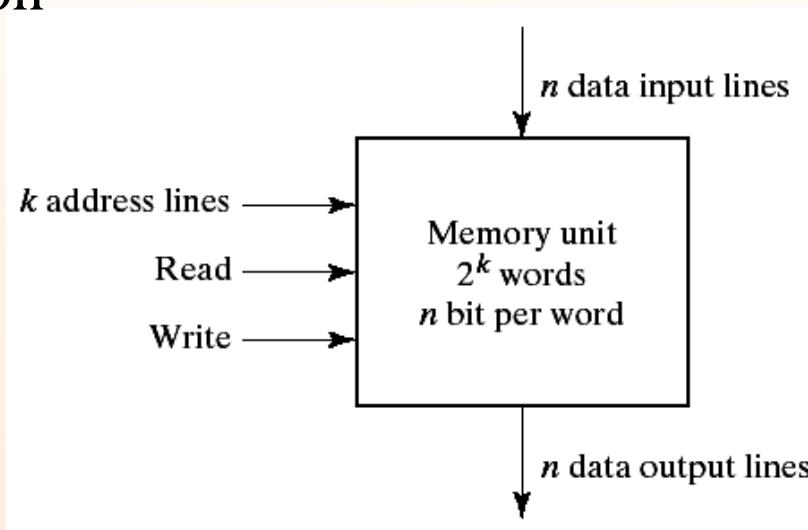
# Mass Memory Elements

□ Memory is a collection of binary cells together with associated circuits needed to transfer information to or from any desired location



- Two primary categories of memory:
  - Random access memory (RAM)
  - Read only memory (ROM)

# Random Access Memory

- ❑ A **word** is the basic unit that moves in and out of memory
  - ❑ The length of a word is often multiples of a byte (=8 bits)
- ❑ Memory units are specified by its **number of words** and the **number of bits in** each word
  - ❑ Ex: 1024(words) x 16(bits)
  - ❑ Each word is assigned a particular **address, starting** from 0 up to  $2^k - 1$  (k = number of address lines)

Memory address		Memory content
Binary	Decimal	
000000000	0	1011010101011101
000000001	1	1010101110001001
000000010	2	0000110101000110
	⋮	⋮
111111101	1021	1001110100010100
111111110	1022	0000110100011110
111111111	1023	1101111000100101


FIGURE 7.3: Contents of a 1024 \* 16 memory

# Write and Read Operations

- ❑ Write to RAM
  - ❑ Apply the binary address of the desired word to the **address lines**
  - ❑ Apply the data bits that must be stored in memory to the **data input lines**
  - ❑ Activate the **write control**
- ❑ Read from RAM
  - ❑ Apply the binary address of the desired word to the **address lines**
  - ❑ Activate the **read control**
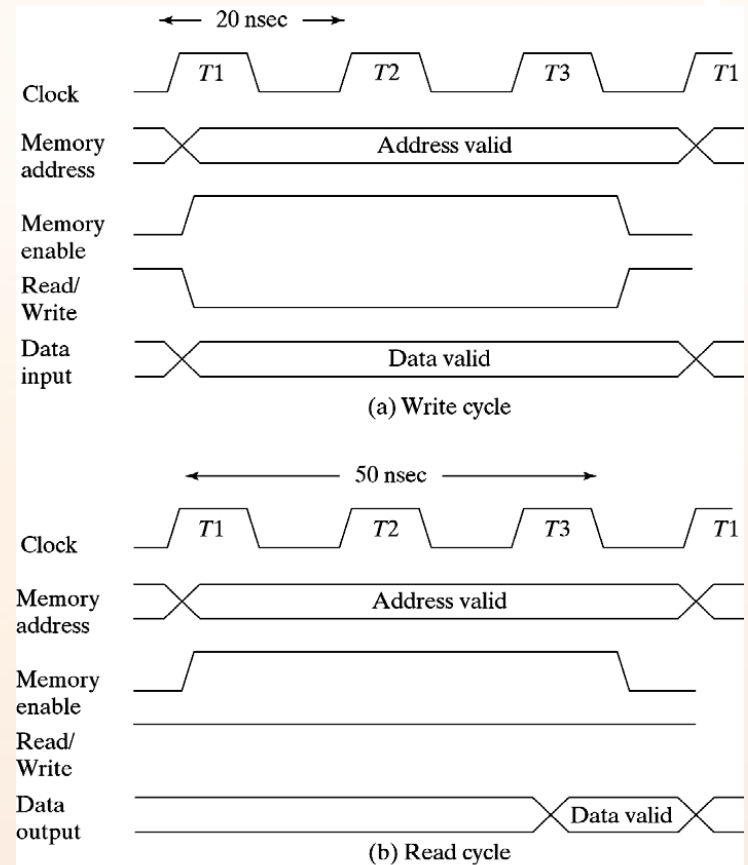
# Timing Waveforms

- ❑ CPU clock = 50 MHz
- ❑ cycle time = 20 ns
- ❑ Memory access time = 50 ns
- ❑ The time required to complete a read or write operation
- ❑ The control signals must stay active for at least 50 ns
- ❑ 3 CPU cycles are required



# Types of Memories

- ❑ Access mode:
  - ❑ Random access: any locations can be accessed in any order
  - ❑ Sequential access: accessed only when the requested word has been reached (ex: hard disk)
- ❑ Operating mode:
  - ❑ Static RAM (SRAM)
  - ❑ Dynamic RAM (DRAM)
- ❑ Volatile mode:
  - ❑ Volatile memory: lose stored information when power is turned off (ex: RAM)
  - ❑ Non-volatile memory: retain its storage after removal of power (ex: flash, ROM, hard-disk, .)



# SRAM vs. DRAM

## ❑ Static RAM:

- ❑ Use internal latch to store the binary information
- ❑ Stored information remains valid as long as power is on
- ❑ Shorter read and write cycles
- ❑ Larger cell area and power consumption


 



Fig. 6-5 Static RAM Cell
 
## ❑ Dynamic RAM:

- ❑ Use a capacitor to store the binary information
- ❑ Need periodically refreshing to hold the stored info.
- ❑ Longer read and write cycles
- ❑ Smaller cell area and power consumption



(a)

 

(h)

# reading

- M. Morris Mano , Michael D. Ciletti "Digital Design With an Introduction to the Verilog HDL" FIFTH EDITION
  - Sections: 6.1 ,6.2(pages 255-259,266-275,280-281)
  - Sections: 7.1 ,7.2(pages 299-302)